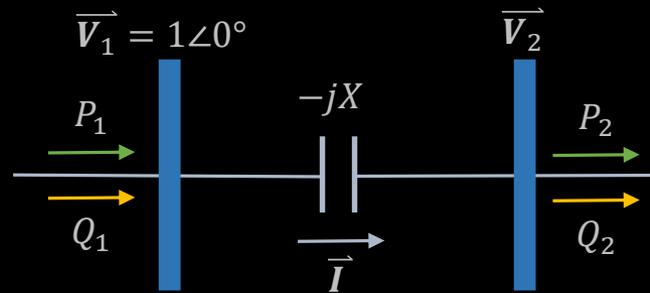


# Series Capacitor Voltage Rise Equations



$$I = \frac{1 - V_2}{-jX} = \frac{1 - |V_2|e^{j\theta_2}}{-jX}$$

$$I = \frac{j - j|V_2|e^{j\theta_2}}{X}$$

$$IX = j - j|V_2|e^{j\theta_2}$$

$$IX = j - |V_2|e^{j\theta_2}e^{j90}$$

$$IX = j - |V_2|e^{j(\theta_2+90)}$$

$$IX = j - |V_2|[\cos(\theta_2 + 90) + j \sin(\theta_2 + 90)]$$

$$IX = j - |V_2|[-\sin \theta_2 + j \cos \theta_2]$$

$$IX = j + |V_2|[\sin \theta_2 - j \cos \theta_2]$$


$$IX = j + |V_2| \sin \theta_2 - j|V_2| \cos \theta_2$$

$$IX = |V_2| \sin \theta_2 + j - j|V_2| \cos \theta_2$$

$$IX = |V_2| \sin \theta_2 + j[1 - |V_2| \cos \theta_2]$$

$$I = \frac{|V_2|}{X} \sin \theta_2 + j \left[ \frac{1 - |V_2| \cos \theta_2}{X} \right]$$
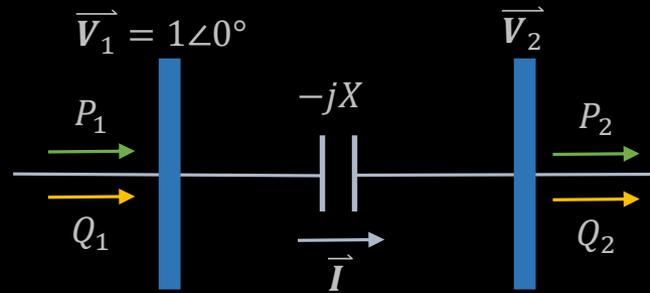
# Series Capacitor Voltage Rise Equations



$$S_1 = V_1 I^* = 1\angle 0^\circ I^* = I^*$$

$$S_1^* = I$$

$$S_1^* = I$$

$$P_1 - jQ_1 = \frac{|V_2|}{X} \sin \theta_2 + j \left[ \frac{1 - |V_2| \cos \theta_2}{X} \right]$$

$$P_1 = \frac{|V_2|}{X} \sin \theta_2$$

$$Q_1 = \frac{|V_2| \cos \theta_2 - 1}{X}$$

$$Q_1 X = |V_2| \cos \theta_2 - 1$$

$$Q_1 X + 1 = |V_2| \cos \theta_2$$

$$|V_2| = \frac{Q_1 X + 1}{\cos \theta_2}$$

$$\Delta V = |V_2| - |V_1| = |V_2| - 1$$

$$\Delta V = \frac{Q_1 X + 1}{\cos \theta_2} - 1$$

$$S_1^* = I$$

$$P_1 - jQ_1 = \frac{1 - V_2}{-jX} = \frac{V_2 - 1}{jX}$$

$$jP_1 X + Q_1 X = V_2 - 1$$

$$V_2 = (Q_1 X + 1) + jP_1 X$$

$$|V_2| = \sqrt{(Q_1 X + 1)^2 + (P_1 X)^2}$$

$$\theta_2 = \tan^{-1} \left[ \frac{P_1 X}{Q_1 X + 1} \right]$$

$$|V_2| = \sqrt{(Q_1 X + 1)^2 + (P_1 X)^2}$$


$$\theta_2 = \tan^{-1} \left[ \frac{P_1 X}{Q_1 X + 1} \right]$$

if  $\theta_2$  is small:

$$\Delta V \approx Q_1 X$$

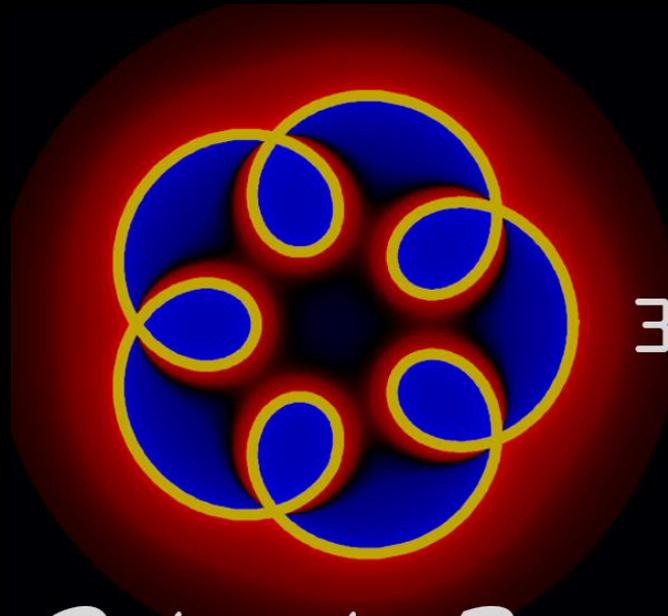series capacitor reactance ( $X$ ) is a positive value





IEE

*Dedicated to Power Engineering*

Questions or Comments ...

[contact us](#)