

YN-yn-d Xfmr in Zero Sequence

use three (3) single phase ideal Xfmrs
 reference pri and sec windings to neutral
 connect tertiary windings as delta
 model pri, sec, ter impedances in series with windings
 add a zero sequence source to primary windings
 short the secondary windings to neutral
 all quantities are per-unit
 when using per-unit system for analysis:

$$V_p = V_s = V_t = V_{source} - I_p^0 Z_p^0 = 1 - I_p^0 Z_p^0$$

because $P_{in} = P_{out}$
 $I_p^0 = I_s^0 + I_t^0$

we are wanting the phase impedance
 "seen" by the source voltage: Z_{in}^0

on the primary side:

$$Z_{in}^0 = \frac{V_{source}}{I_p^0} = \frac{1}{I_p^0}$$

$$I_p^0 = \frac{1}{Z_{in}^0}$$


on the secondary side:

$$I_s^0 = \frac{V_s}{Z_s^0} = \frac{1 - I_p^0 Z_p^0}{Z_s^0}$$

on the tertiary side:

$$I_t^0 = \frac{V_t}{Z_t^0} = \frac{1 - I_p^0 Z_p^0}{Z_t^0}$$

$$V_{source} = 1 \angle 0^\circ$$

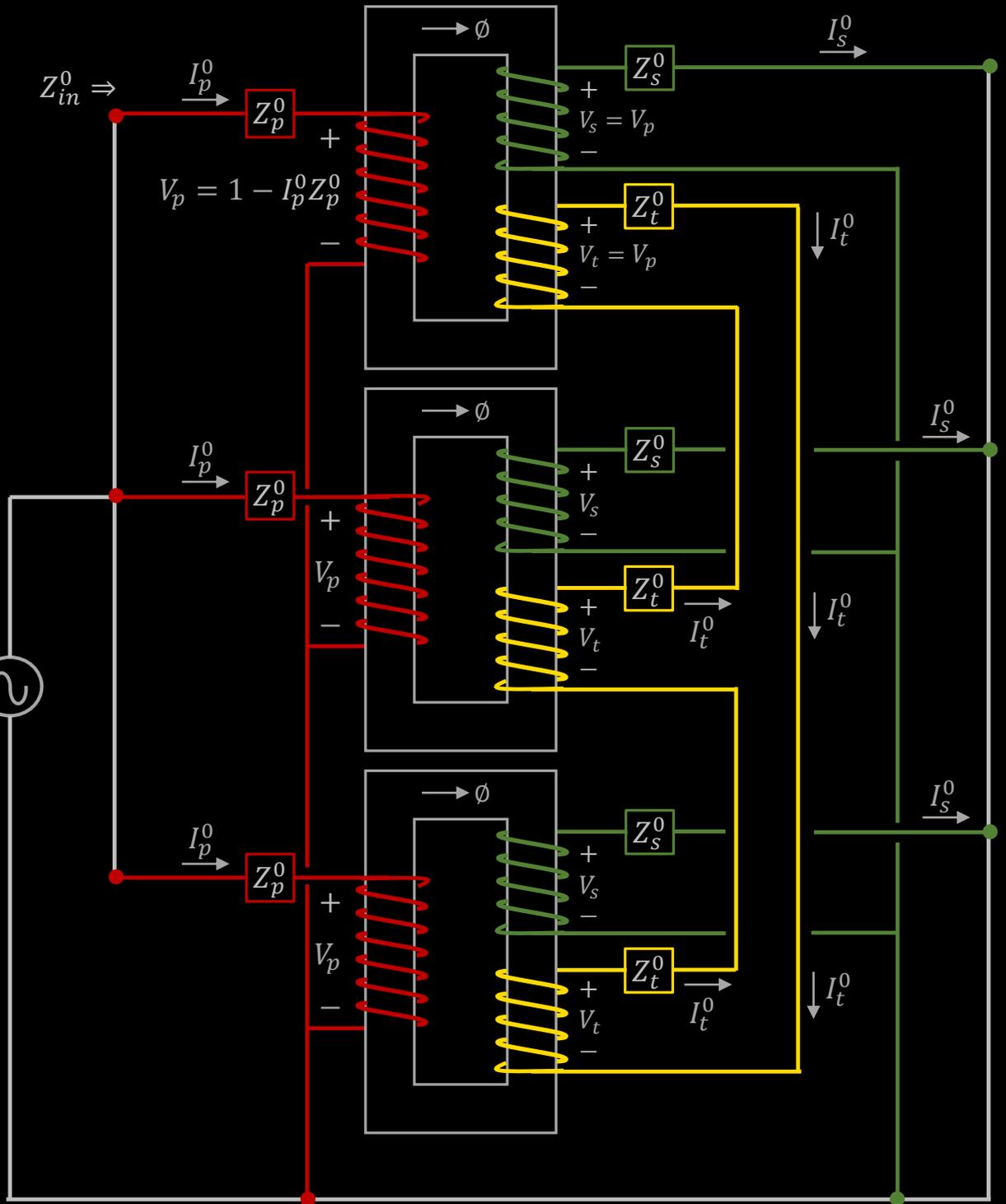YN-yn-d Xfmr in Zero Sequence

because $P_{in} = P_{out}$

$$I_p^0 = I_s^0 + I_t^0$$

$$I_p^0 = \frac{1 - I_p^0 Z_p^0}{Z_s^0} + \frac{1 - I_p^0 Z_p^0}{Z_t^0}$$

$$I_p^0 = \frac{1}{Z_s^0} - \frac{I_p^0 Z_p^0}{Z_s^0} + \frac{1}{Z_t^0} - \frac{I_p^0 Z_p^0}{Z_t^0}$$

$$I_p^0 + \frac{I_p^0 Z_p^0}{Z_s^0} + \frac{I_p^0 Z_p^0}{Z_t^0} = \frac{1}{Z_s^0} + \frac{1}{Z_t^0}$$

$$I_p^0 \left[1 + \frac{Z_p^0}{Z_s^0} + \frac{Z_p^0}{Z_t^0} \right] = \frac{1}{Z_s^0} + \frac{1}{Z_t^0}$$

$$I_p^0 = \frac{\left[\frac{1}{Z_s^0} + \frac{1}{Z_t^0} \right]}{\left[1 + \frac{Z_p^0}{Z_s^0} + \frac{Z_p^0}{Z_t^0} \right]}$$

$$I_p^0 = \frac{\left[\frac{1}{Z_s^0} + \frac{1}{Z_t^0} \right] Z_s^0 Z_t^0}{\left[1 + \frac{Z_p^0}{Z_s^0} + \frac{Z_p^0}{Z_t^0} \right] Z_s^0 Z_t^0}$$

$$I_p^0 = \frac{Z_t^0 + Z_s^0}{Z_s^0 Z_t^0 + Z_p^0 Z_t^0 + Z_p^0 Z_s^0}$$

$$Z_{in}^0 = \frac{1}{I_p^0} = \frac{Z_s^0 Z_t^0 + Z_p^0 Z_t^0 + Z_p^0 Z_s^0}{Z_t^0 + Z_s^0}$$


$$Z_{in}^0 = \frac{Z_s^0 Z_t^0}{Z_s^0 + Z_t^0} + \frac{Z_p^0 [Z_s^0 + Z_t^0]}{Z_s^0 + Z_t^0}$$

$$Z_{in}^0 = Z_p^0 + \frac{Z_s^0 Z_t^0}{Z_s^0 + Z_t^0}$$

$$Z_{in}^0 = Z_p^0 + Z_s^0 \parallel Z_t^0$$

$$Z_{in}^0 = Z_p^0 + Z_s^0 \parallel Z_t^0$$

$V_{source} = 1 \angle 0^\circ$

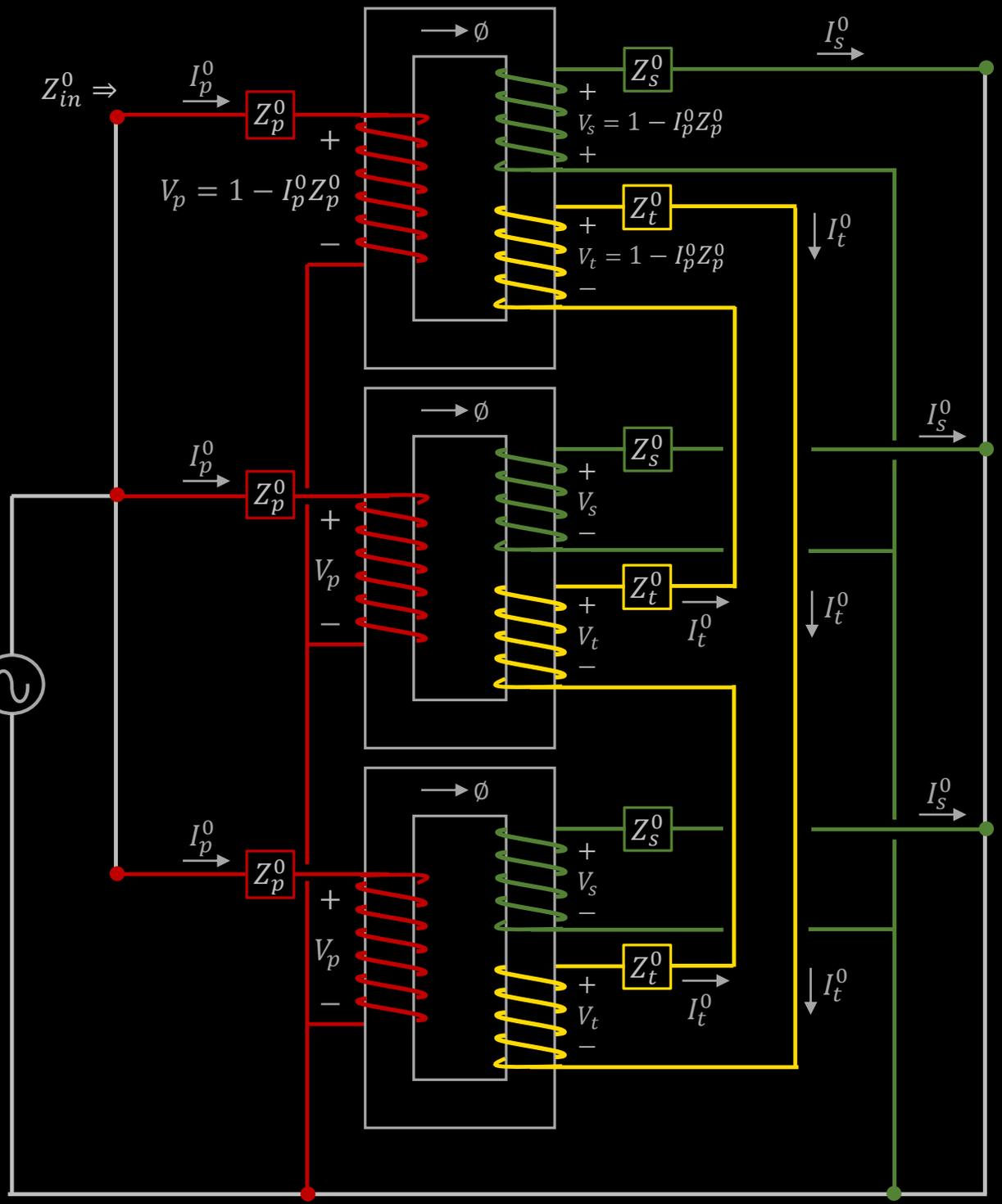


YN-yn-d Xfmr in Zero Sequence


$$Z_{in}^0 = Z_p^0 + Z_s^0 \parallel Z_t^0 \Rightarrow$$

the results of this derivation reveal that the zero sequence impedance of the delta tertiary is effectively connected to the neutral !! this is not intuitive when looking at the electrical circuit. (notice the circulating current in the delta tertiary)

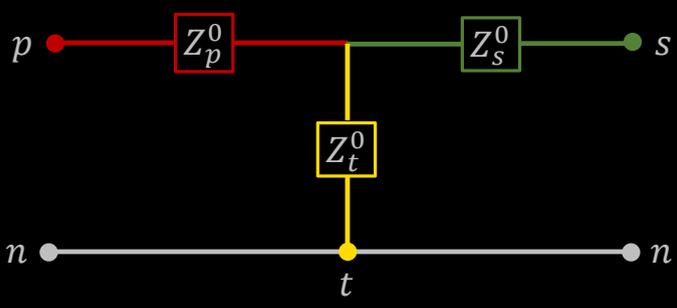So when performing a per-phase analysis in zero sequence, the YYΔ transformer T-model looks like this:



$$V_{source} = 1 \angle 0^\circ$$

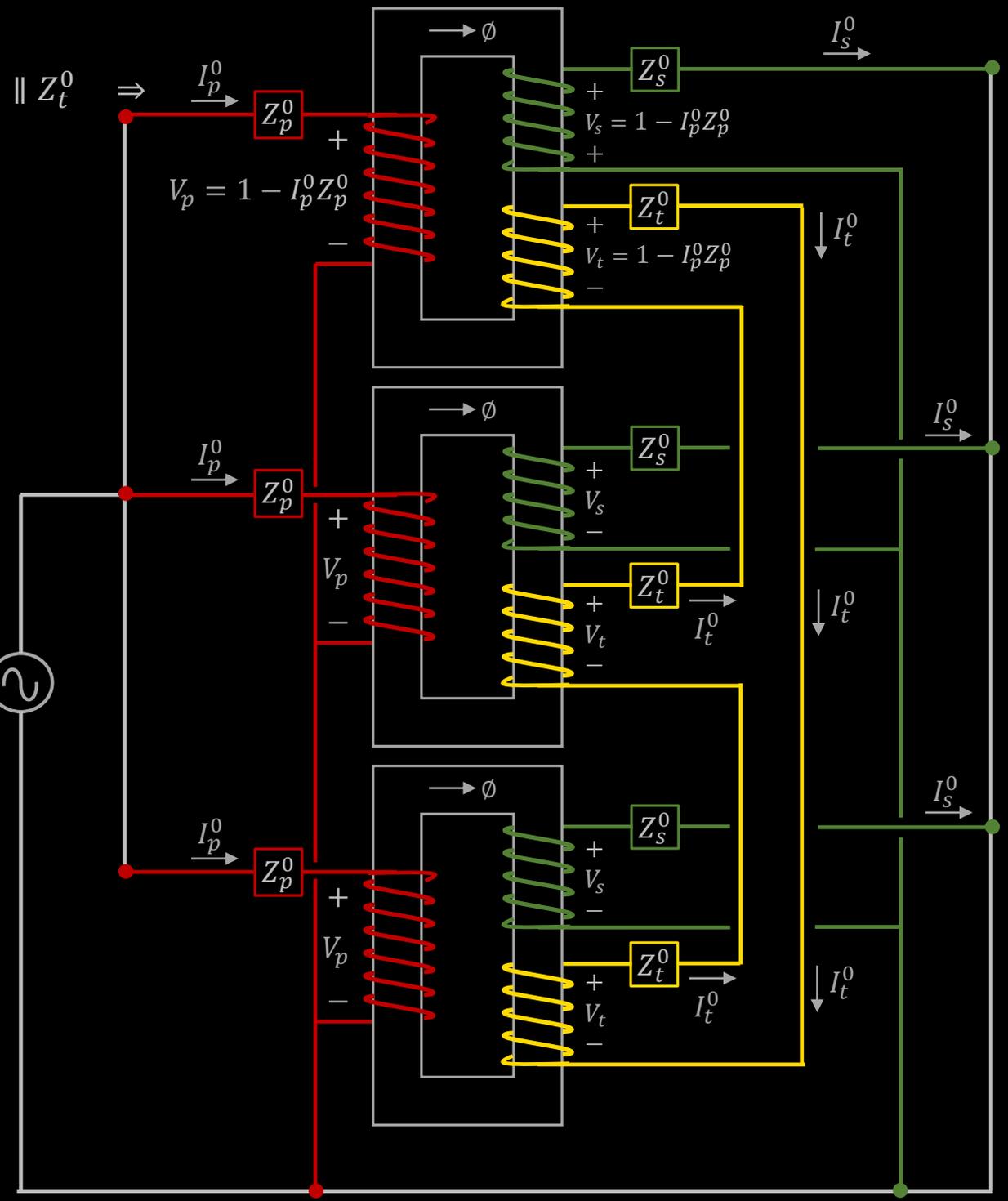



ΕΦΕΕ

Dedicated to Power Engineering

Questions or Comments ...

[contact us](#)